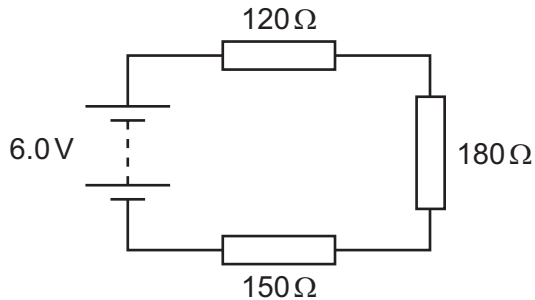


- 37** Three resistors are connected in series with a battery, as shown. The battery has negligible internal resistance.



What is the potential difference across the 180 Ω resistor?

- A** 1.6 V                      **B** 2.4 V                      **C** 3.6 V                      **D** 4.0 V