

31 Which values of current and resistance will produce a rate of energy transfer of 16 J s^{-1} ?

	current / A	resistance / Ω
A	1	4
B	2	8
C	4	1
D	16	1

32 A cylindrical wire 4.0 m long has a resistance of 21Ω and is made of metal of resistivity