

- 5 (a) On Fig. 5.1, sketch the temperature characteristic of a thermistor.

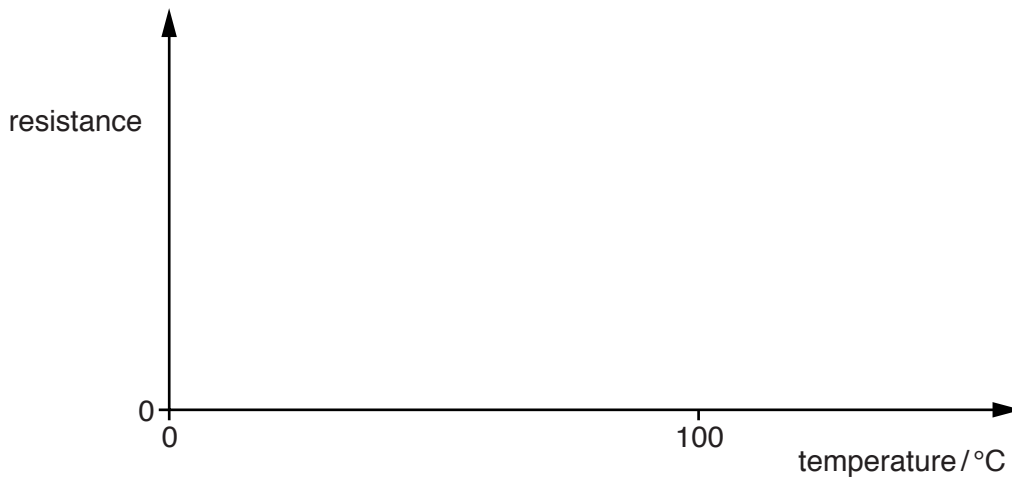


Fig. 5.1

[2]

- (b) A potential divider circuit is shown in Fig. 5.2.

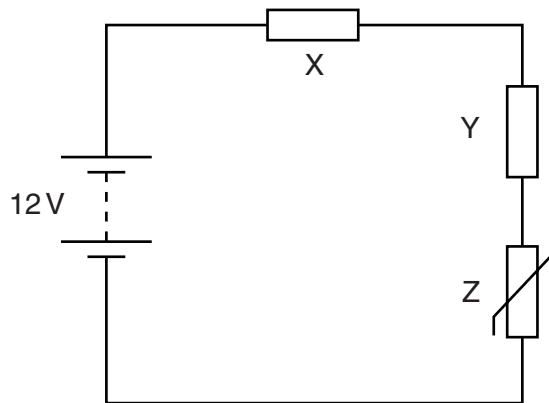


Fig. 5.2

The battery of electromotive force (e.m.f.) 12 V and negligible internal resistance is connected in series with resistors X and Y and thermistor Z. The resistance of Y is $15\text{ k}\Omega$ and the resistance of Z at a particular temperature is $3.0\text{ k}\Omega$. The potential difference (p.d.) across Y is 8.0 V.

- (i) Explain why the power transformed in the battery equals the total power transformed in X, Y and Z.

..... [1]

- (ii) Calculate the current in the circuit.

current = A [2]

- (iii) Calculate the resistance of X.

resistance = Ω [3]

- (iv) The temperature of Z is increased.

State and explain the effect on the potential difference across Z.

.....
.....
.....
..... [2]