

- 5 (a) (i) State what is meant by an *electric current*.

.....
 [1]

- (ii) Define electric *potential difference* (*p.d.*).

.....
 [1]

- (b) A power supply of electromotive force (e.m.f.) 8.7 V and negligible internal resistance is connected by two identical wires to three filament lamps, as shown in Fig. 5.1.

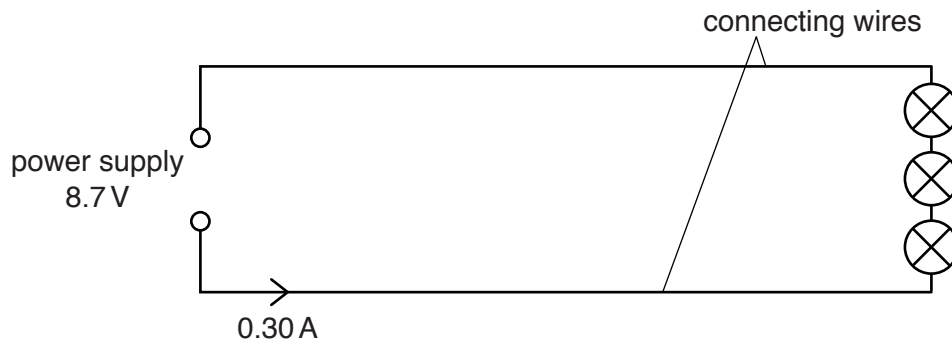


Fig. 5.1 (not to scale)

The power supply provides a current of 0.30 A to the circuit.
 The filament lamps are identical. The I – V characteristic for **one** of the lamps is shown in Fig. 5.2.

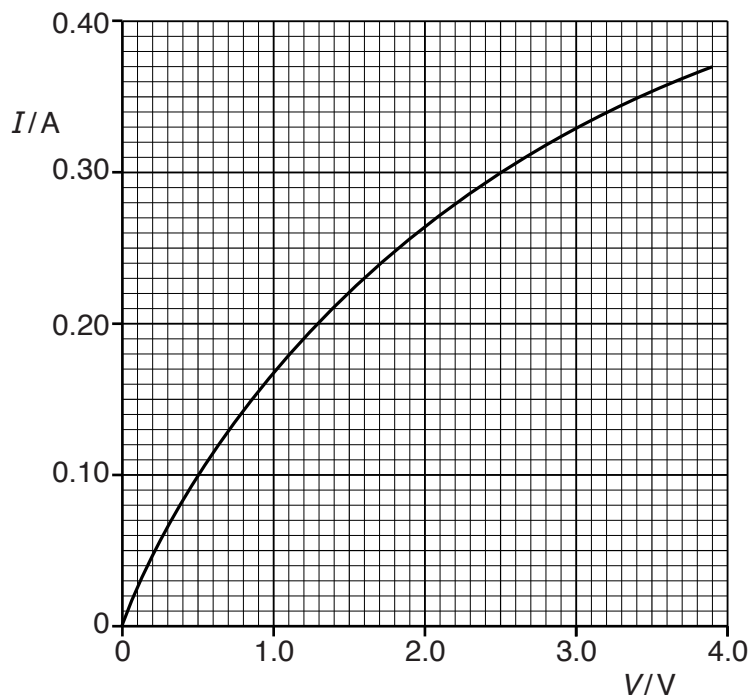


Fig. 5.2

- (i) Show that the resistance of each connecting wire is $2.0\ \Omega$.

[2]

- (ii) The resistivity of the metal of the connecting wires does not vary with temperature. On Fig. 5.2, sketch the I - V characteristic for **one** of the connecting wires.

[2]

- (iii) Calculate the power loss in one of the connecting wires.

power = W [2]

- (iv) Some data for the connecting wires are given below.

cross-sectional area = 0.40 mm^2 resistivity = $1.7 \times 10^{-8}\ \Omega\text{ m}$ number density of free electrons = $8.5 \times 10^{28}\text{ m}^{-3}$

Calculate

1. the length of one of the connecting wires,

length = m [2]

2. the drift speed of a free electron in the connecting wires.

drift speed = ms^{-1} [2]

[Total: 12]