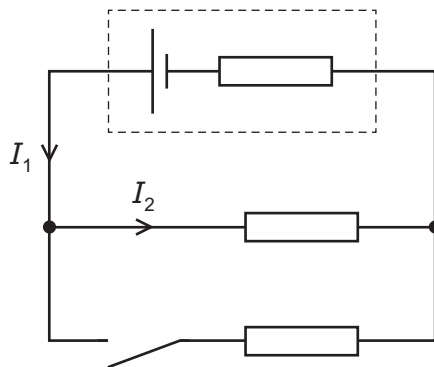


35 The diagram shows a circuit that includes a cell with internal resistance.



The switch is initially open.

Which row describes the effects on currents I_1 and I_2 of closing the switch?

	I_1	I_2
A	decreases	decreases
B	decreases	stays the same
C	increases	decreases
D	increases	stays the same