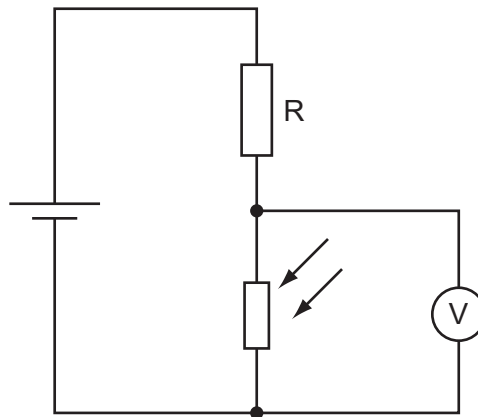


32 A potential divider consists of a fixed resistor R and a light-dependent resistor (LDR).



What happens to the voltmeter reading, and why does it happen, when the intensity of light on the LDR increases?

- A** The voltmeter reading decreases because the LDR resistance decreases.
- B** The voltmeter reading decreases because the LDR resistance increases.
- C** The voltmeter reading increases because the LDR resistance decreases.
- D** The voltmeter reading increases because the LDR resistance increases.