

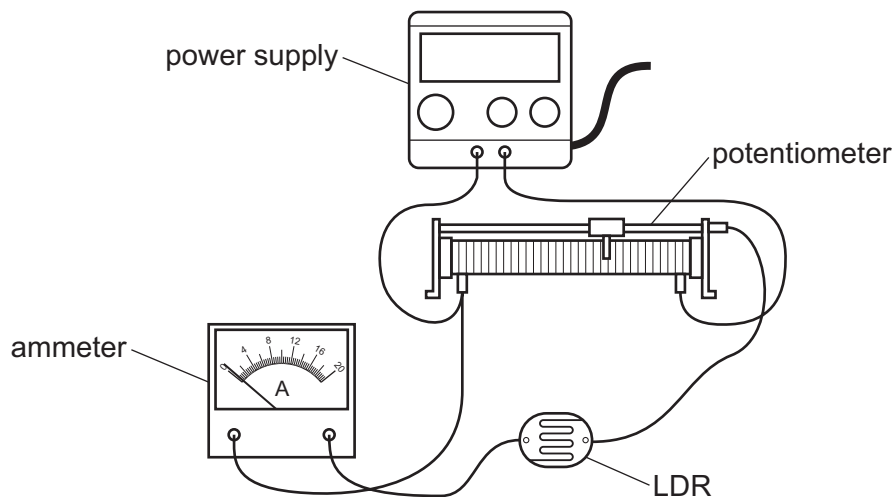
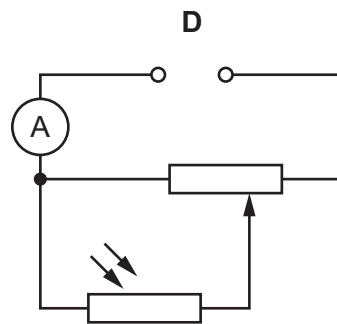
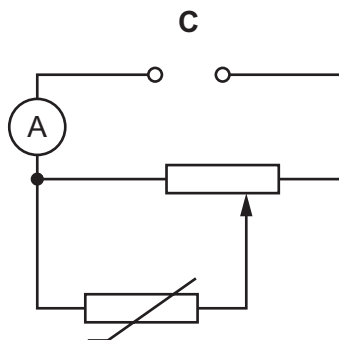


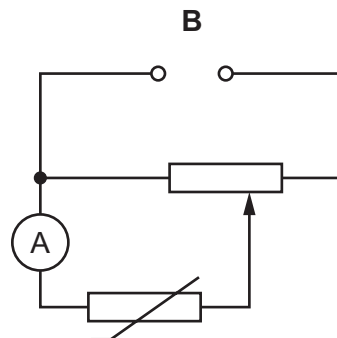33 The diagram shows an electrical circuit containing a light-dependent resistor (LDR).



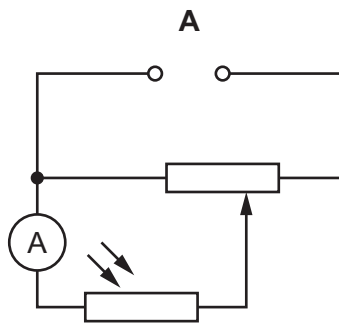What is the circuit diagram for this circuit?



34 A copper wire of length 2 m has a circular cross section. There is a constant current in the wire