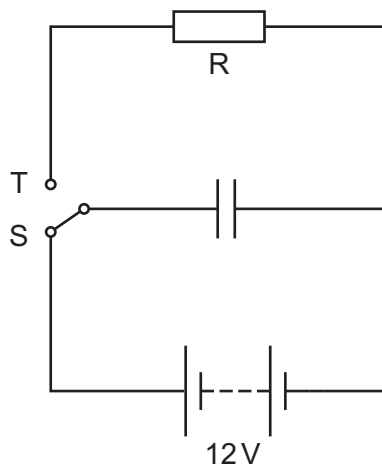



- 5 A capacitor, a battery of electromotive force (e.m.f.) 12V, a resistor R and a two-way switch are connected in the circuit shown in Fig. 5.1.



**Fig. 5.1**

The switch is initially in position S. When the capacitor is fully charged, the switch is moved to position T so that the capacitor discharges. At time  $t$  after the switch is moved the charge on the capacitor is  $Q$ .

The variation with  $t$  of  $\ln(Q/\mu\text{C})$  is shown in Fig. 5.2.

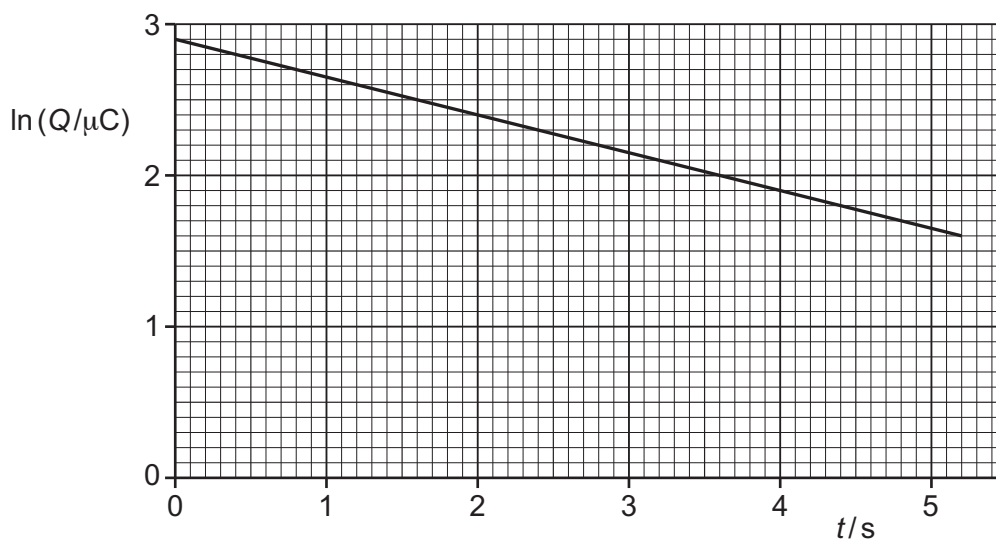

**Fig. 5.2**

- (a) Show that the capacitance of the capacitor is  $1.5\mu\text{F}$ .

- (b) Determine the resistance of R.

resistance = .....  $\Omega$  [3]

- (c) Calculate the energy stored in the capacitor at time  $t = 0$ .

energy = ..... J [2]

- (d) A second identical resistor is now connected in parallel with R.

The switch is initially in position S. When the capacitor is fully charged, the switch is moved to position T so that the capacitor discharges. At time  $t$  after the switch is moved the charge on the capacitor is  $Q$ .

On Fig. 5.2, sketch a line to show the variation of  $\ln(Q/\mu\text{C})$  with  $t$  between time  $t = 0$  and time  $t = 5.0\text{ s}$ . [2]