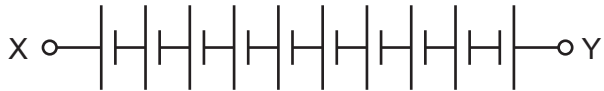


- 33** Ten cells, each of electromotive force (e.m.f.) 1.5 V , are connected together, as shown.



What is the combined e.m.f. between terminals X and Y?

A 8 V

B 9 V

C 12 V

D 15 V