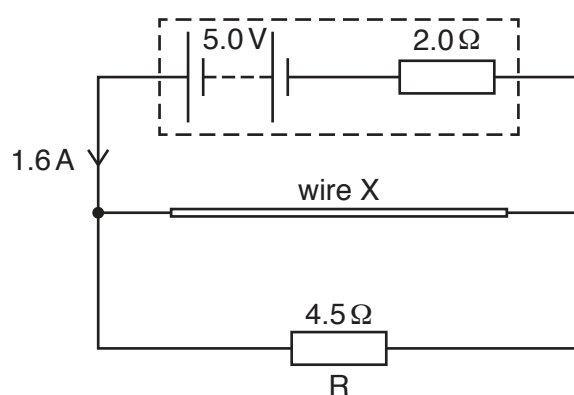


- 6 A wire X has a constant resistance per unit length of  $3.0\ \Omega\text{m}^{-1}$  and a diameter of 0.48 mm.

(a) Calculate the resistivity of the metal of wire X.

resistivity = .....  $\Omega\text{m}$  [3]

(b) The wire X is connected into the circuit shown in Fig. 6.1.



**Fig. 6.1**

The battery has an electromotive force (e.m.f.) of 5.0 V and an internal resistance of  $2.0\ \Omega$ . The wire X and a resistor R of resistance  $4.5\ \Omega$  are connected in parallel. The current in the battery is 1.6 A.

(i) Calculate the potential difference across resistor R.

potential difference = ..... V [1]

(ii) Determine, for wire X,

1. its resistance,

resistance = .....  $\Omega$  [3]

2. its length.

length = ..... m [1]

[Total: 8]

**Please turn over for Question 7.**