

**37** In the circuits shown, the temperature remains constant.

In which circuit does the potential difference (p.d.)  $V$  increase with increasing light intensity?

