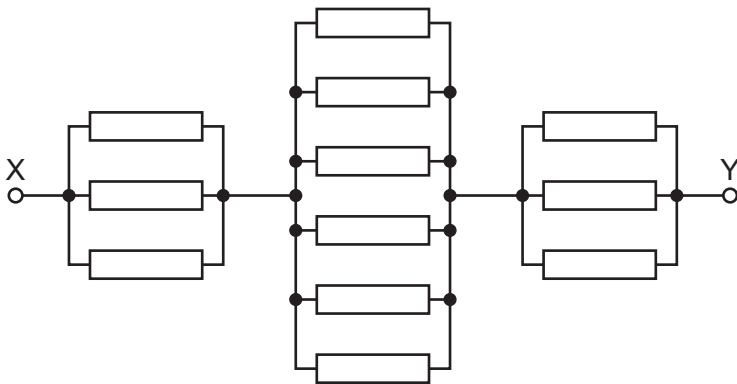


36 The diagram shows a network of resistors. Each resistor has a resistance of $6.0\ \Omega$.



What is the total resistance of the network between points X and Y?

A $3.0\ \Omega$

B $5.0\ \Omega$

C $7.2\ \Omega$

D $18\ \Omega$