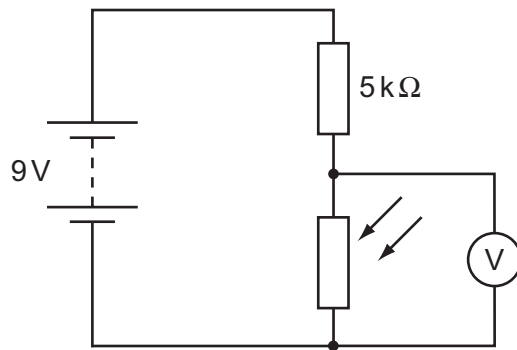


34 A circuit is set up with an LDR and a fixed resistor as shown.



The voltmeter reads 4 V.

The light intensity is increased.

What is a possible voltmeter reading?

A 3 V

B 4 V

C 6 V

D 8 V