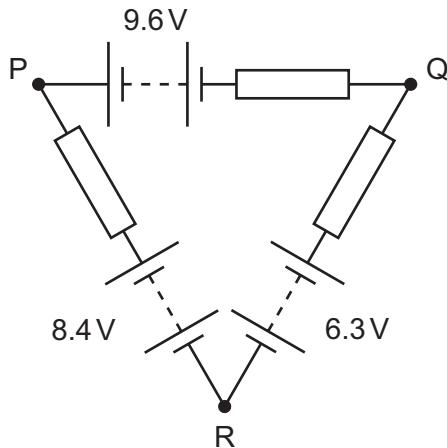


- 36** Three batteries and three identical resistors are connected in a circuit PQR, as shown.



The batteries have negligible internal resistance.

What is the potential difference between points P and Q?

- A** 1.5V                      **B** 2.1V                      **C** 7.1V                      **D** 12.1V