

20 A transformer has the following input and output.

	potential difference / V	current / A
input	11 000	28
output	240	1200

What is the efficiency of the transformer?

A 0.94 %

B 1.0 %

C 11 %

D 94 %

Space for working