

- 34** Which graph best represents the variation with current I of potential difference V for a filament lamp?

