

- 5 (a) A capacitor of capacitance C_1 is connected in series with a second capacitor of capacitance C_2 .

Show that the combined capacitance C of the two capacitors is given by

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}.$$

[2]

- (b) Three identical capacitors, each of capacitance C , are connected in a network as shown in Fig. 5.1.

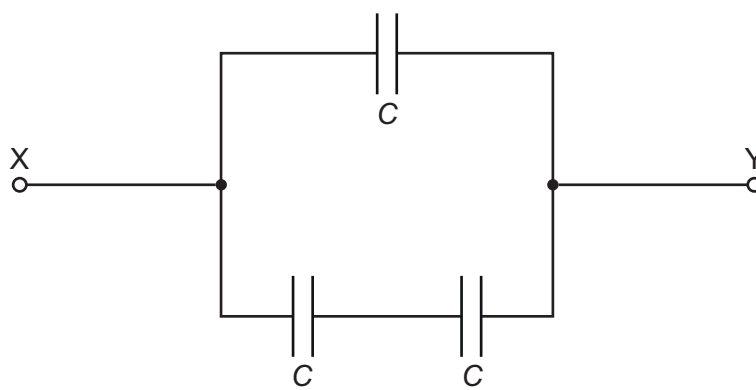


Fig. 5.1

The variation of the charge Q with the potential difference (p.d.) V between the terminals X and Y is shown in Fig. 5.2.

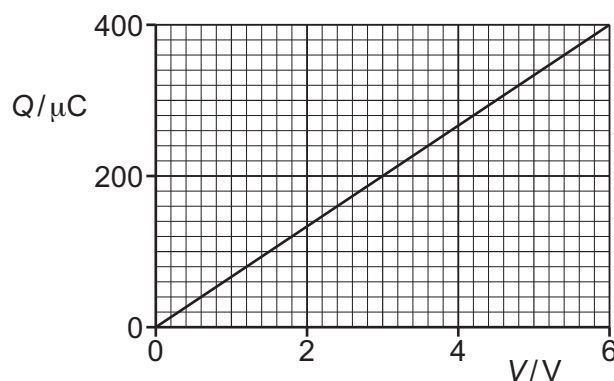


Fig. 5.2





Show that C is equal to $44\mu\text{F}$.

[3]

- (c) The capacitor network in Fig. 5.1 is charged and then connected to a resistor of resistance $54\text{ k}\Omega$. The capacitor network discharges through the resistor.

(i) Determine the time constant τ of the circuit. Give a unit with your answer.

$\tau = \dots\dots\dots$ unit $\dots\dots\dots$ [2]

(ii) Determine the time taken for the discharge current to reduce to 15% of the initial discharge current.

time = $\dots\dots\dots$ s [2]