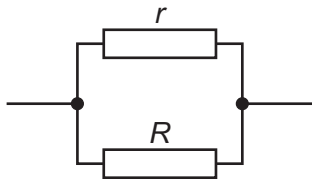


35 Two resistors of resistances r and R are connected in parallel.

The value of r is less than that of R .



Which statement about the combined resistance of the two resistors is correct?

- A** It is between r and R .
- B** It is equal to $(r + R)$.
- C** It is greater than $(r + R)$.
- D** It is less than r .