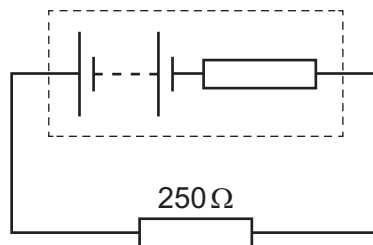


- 31** A battery with a constant internal resistance is connected to a resistor of resistance $250\ \Omega$, as shown.



The current in the resistor is $40\ \text{mA}$ for a time of $60\ \text{s}$. During this time $6.0\ \text{J}$ of energy is dissipated by the internal resistance.

What is the energy supplied to the external resistor during the $60\ \text{s}$ and the electromotive force (e.m.f.) of the battery?

	energy / J	e.m.f. / V
A	30	2.5
B	30	7.5
C	24	10.0
D	24	12.5