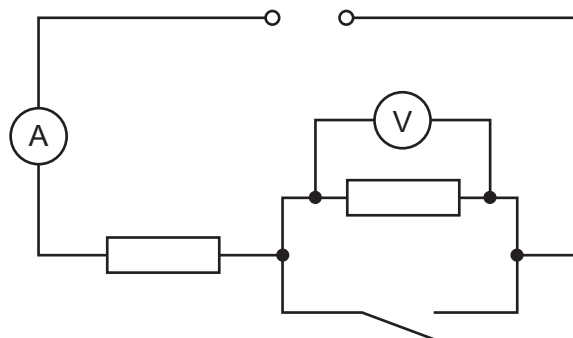


36 In the circuit below, the ammeter reading is I and the voltmeter reading is V .



When the switch is closed, which row describes what happens to I and V ?

	I	V
A	decreases	decreases to zero
B	increases	decreases to zero
C	increases	stays the same
D	stays the same	increases

Space for working