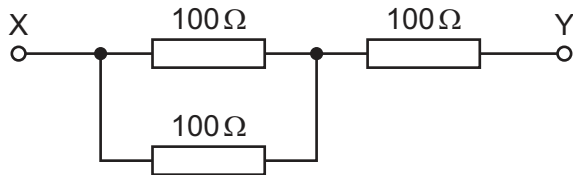


33 Three resistors are to be connected into a circuit with the arrangement shown.



The power in any resistor must not be greater than 4.0 W .

What is the maximum voltage across XY?

A 24 V

B 30 V

C 40 V

D 60 V