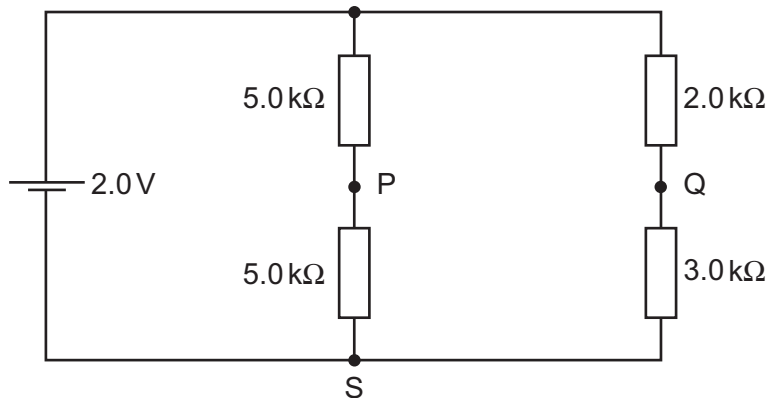


- 33** A cell of e.m.f. 2.0 V and negligible internal resistance is connected to the network of resistors shown.



V_1 is the potential difference between S and P. V_2 is the potential difference between S and Q.

What is the value of $V_1 - V_2$?

- A** $+0.50\text{ V}$ **B** $+0.20\text{ V}$ **C** -0.20 V **D** -0.50 V