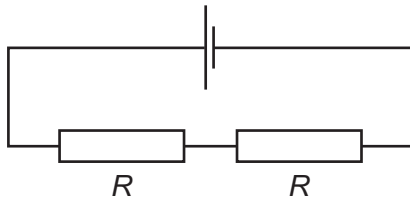
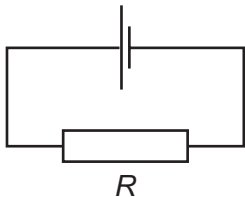


33 The diagrams show two different circuits.



The cells in each circuit have the same electromotive force and zero internal resistance. The three resistors each have the same resistance R .

In the circuit on the left, the power dissipated in the resistor is P .

What is the total power dissipated in the circuit on the right?

A $\frac{P}{4}$

B $\frac{P}{2}$

C P

D $2P$

34 Which equation that links some of the following terms is correct?