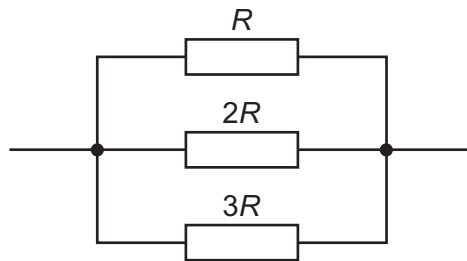


38 Three resistors of resistance R , $2R$ and $3R$ are connected in parallel.



Using I to represent the current through the resistor of resistance R , which row represents the relationships between the currents through the resistors?

	resistor resistance		
	R	$2R$	$3R$
A	I	$\frac{1}{3} I$	$\frac{1}{2} I$
B	I	$\frac{1}{2} I$	$\frac{1}{3} I$
C	I	$\frac{2}{3} I$	$\frac{1}{3} I$
D	I	$2I$	$3I$

Space for working