

- 4 A circuit used to measure the power transfer from a battery is shown in Fig. 4.1. The power is transferred to a variable resistor of resistance R .

For
Examiner's
Use

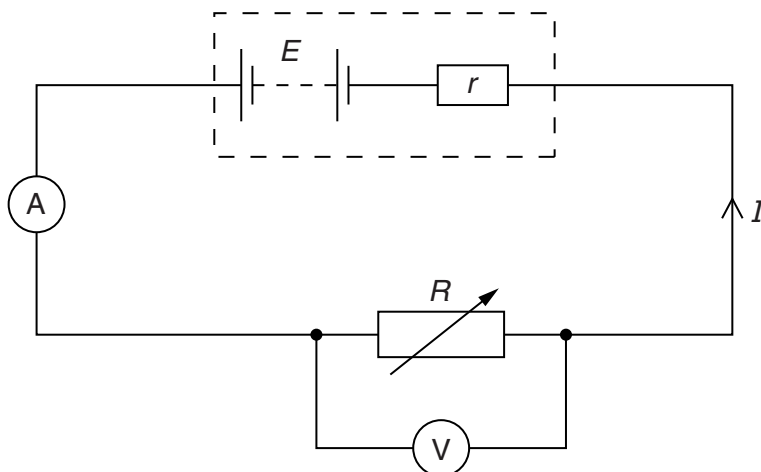


Fig. 4.1

The battery has an electromotive force (e.m.f.) E and an internal resistance r . There is a potential difference (p.d.) V across R . The current in the circuit is I .

- (a) By reference to the circuit shown in Fig. 4.1, distinguish between the definitions of e.m.f. and p.d.

.....

.....

.....

..... [3]

- (b) Using Kirchhoff's second law, determine an expression for the current I in the circuit.

[1]

- (c) The variation with current I of the p.d. V across R is shown in Fig. 4.2.

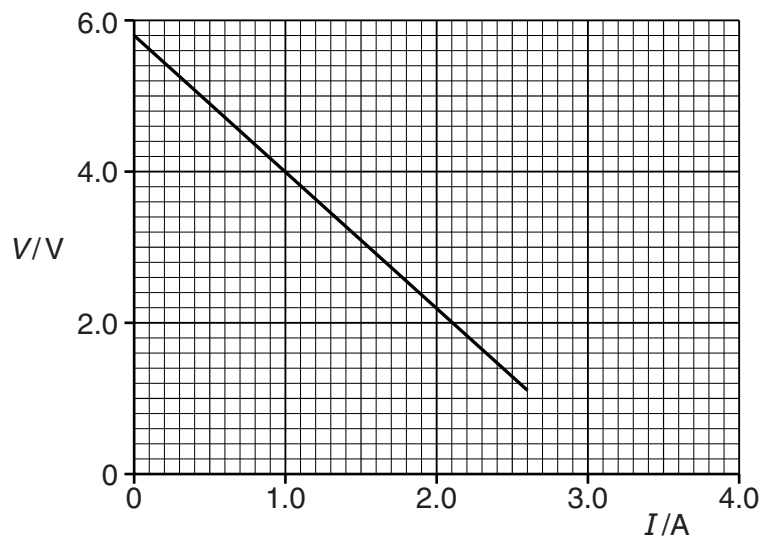


Fig. 4.2

Use Fig. 4.2 to determine

- (i) the e.m.f. E ,

$$E = \dots\dots\dots \text{ V [1]}$$

- (ii) the internal resistance r .

$$r = \dots\dots\dots \Omega \text{ [2]}$$

- (d) (i) Using data from Fig. 4.2, calculate the power transferred to R for a current of 1.6 A.

$$\text{power} = \dots\dots\dots \text{ W [2]}$$

- (ii) Use your answers from (c)(i) and (d)(i) to calculate the efficiency of the battery for a current of 1.6 A.

$$\text{efficiency} = \dots\dots\dots \% \text{ [2]}$$