

- 4 (a) Distinguish between *potential difference* (p.d.) and *electromotive force* (e.m.f.) in terms of energy transformations.

.....

 [2]

- (b) Two cells A and B are connected in series with a resistor R of resistance 5.5Ω , as shown in Fig. 4.1.

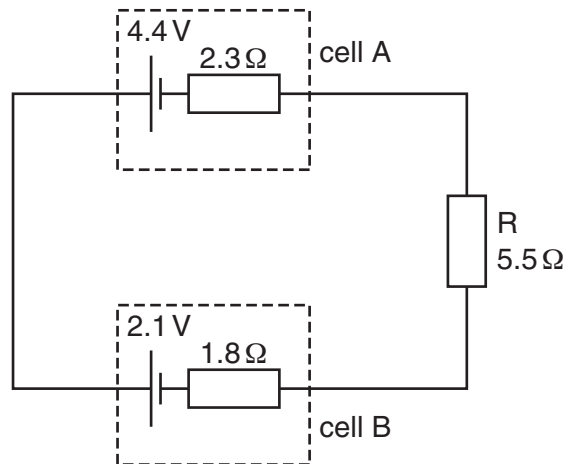


Fig. 4.1

Cell A has e.m.f. 4.4 V and internal resistance 2.3Ω . Cell B has e.m.f. 2.1 V and internal resistance 1.8Ω .

- (i) State Kirchhoff's second law.

.....
 [1]

- (ii) Calculate the current in the circuit.

current = A [2]

- (iii) On Fig. 4.1, draw an arrow to show the direction of the current in the circuit. Label this arrow *I*. [1]

(iv) Calculate

For
Examiner's
Use

1. the p.d. across resistor R,

p.d. = V [1]

2. the terminal p.d. across cell A,

p.d. = V [1]

3. the terminal p.d. across cell B.

p.d. = V [2]