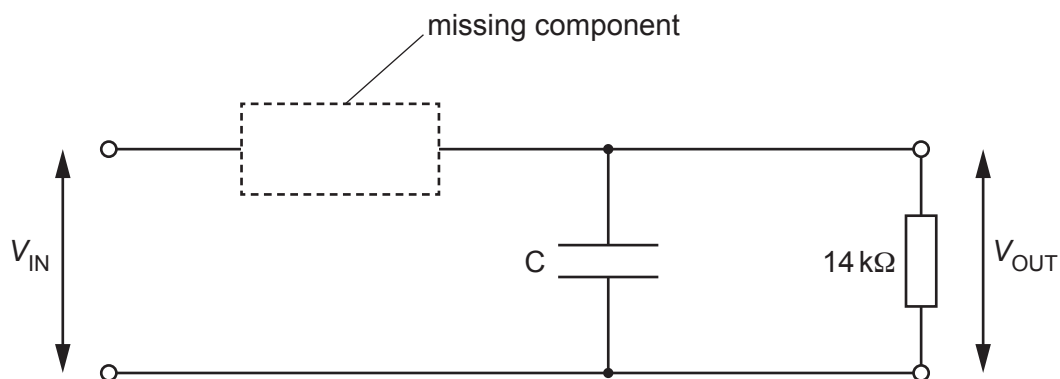


- 5 Part of an electric circuit is shown in Fig. 5.1.



**Fig. 5.1**

The circuit is used to produce half-wave rectification of an alternating voltage of potential difference (p.d.)  $V_{IN}$ .

The output p.d. across the  $14\text{ k}\Omega$  resistor is  $V_{OUT}$ .

- (a) (i) A component is missing from the circuit of Fig. 5.1.


Complete the circuit diagram in Fig. 5.1 by adding the circuit symbol for the missing component, correctly connected. [1]

- (ii) A capacitor  $C$  is shown in the circuit of Fig. 5.1.

State the effect on  $V_{OUT}$  of including the capacitor in the circuit.


..... [1]

- (b) Fig. 5.2 shows the variation with time  $t$  of  $V_{IN}$ .

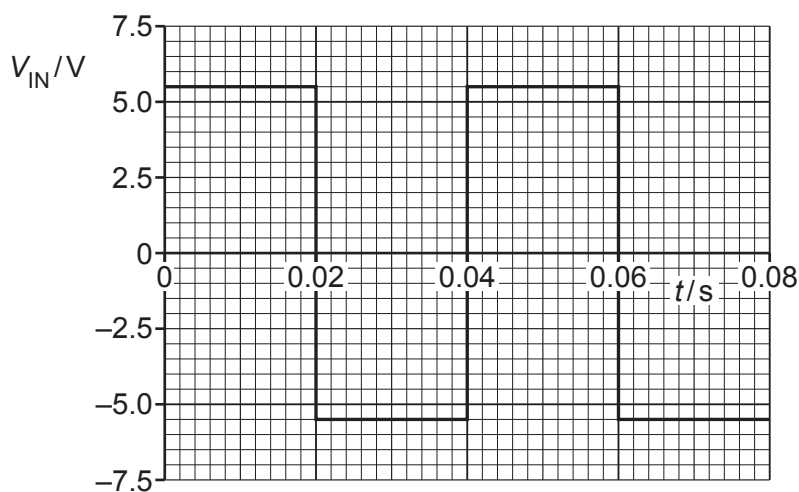

**Fig. 5.2**

Fig. 5.3 shows the variation with  $t$  of  $V_{OUT}$ .

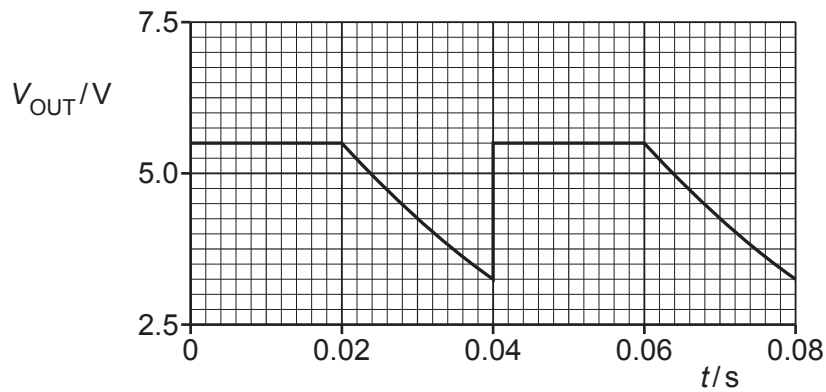

**Fig. 5.3**

- (i) Determine the frequency of  $V_{IN}$ .

frequency = ..... Hz [1]

- (ii) Show that the time constant  $\tau$  for the discharge of the capacitor through the resistor is 0.038s.

[2]

- (iii) Calculate the capacitance of C. Give a unit with your answer.

capacitance = ..... unit ..... [2]

- (c) The circuit of Fig. 5.1 is modified so that it produces full-wave rectification of an input voltage. Suggest, with a reason, how  $V_{OUT}$  now varies with time when  $V_{IN}$  is as shown in Fig. 5.2.

.....  
 .....  
 ..... [2]