

- 33** The terminal voltage of a battery is observed to fall when the battery supplies a current to an external resistor.

What quantities are needed to calculate the fall in voltage?

- A** the battery's e.m.f. and its internal resistance
- B** the battery's e.m.f. and the current
- C** the current and the battery's internal resistance
- D** the current and the external resistance