

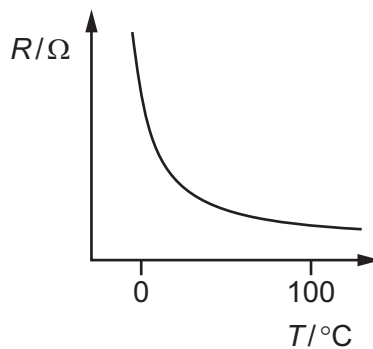
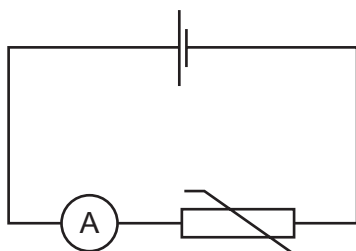
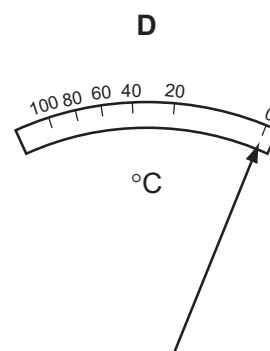
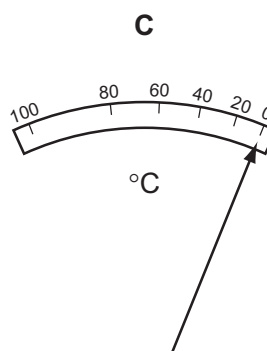


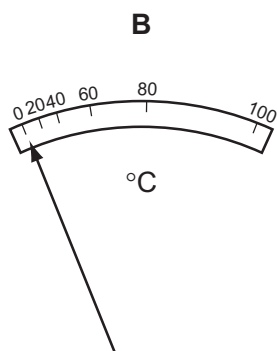- 3 In the circuit shown, an analogue ammeter is to be recalibrated as a thermometer. The graph shows how the resistance  $R$  of the thermistor changes with temperature  $T$ .



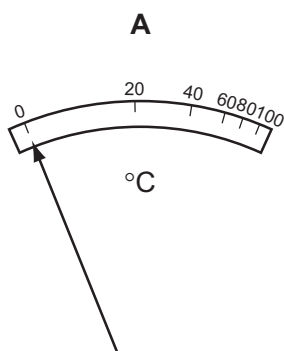Which diagram could represent the temperature scale on the ammeter?



Space for working