

**33** An electric kettle is marked 3.10 kW. It is used with an electrical supply of 240 V.

What is the electric current in the kettle and what is the kettle's electrical resistance when working?

	current / A	resistance / $\Omega$
<b>A</b>	0.0129	18 600
<b>B</b>	0.0770	3100
<b>C</b>	12.9	18.6
<b>D</b>	12.9	3100

**34** A thin wire is used to make a resistor. The wire has a diameter of 0.25 mm and a length of 1.0 m. The wire is made of a material with a resistivity of  $1.1 \times 10^{-8} \Omega \text{ m}$ .