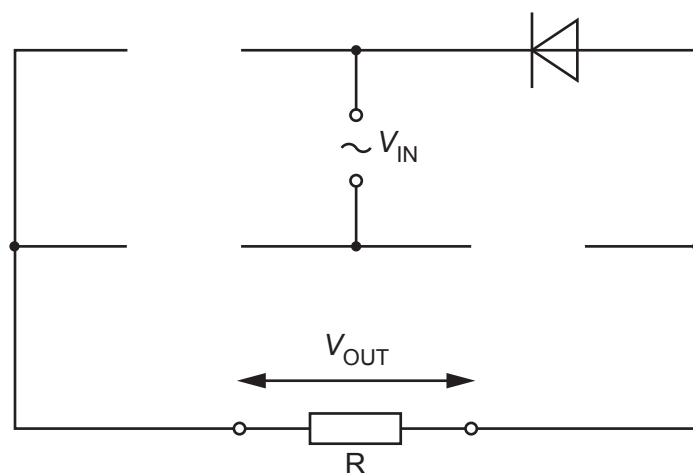



- 7 Four diodes are used in a bridge rectifier circuit to produce rectification of a sinusoidal a.c. input voltage  $V_{IN}$ .  
Fig. 7.1 shows part of the circuit, but three of the diodes are missing.



**Fig. 7.1**


The p.d. across the load resistor  $R$  is the output p.d.  $V_{OUT}$  of the bridge rectifier.

- (a) (i) State the name of the type of rectification produced by a bridge rectifier. [1]  
.....
- (ii) Complete Fig. 7.1 by drawing the three missing diodes, correctly connected. [2]
- (iii) On Fig. 7.1, draw an arrow to indicate the direction of the current in resistor  $R$ . [1]
- (b)  $V_{IN}$  has amplitude  $V_0$  and period  $T$ . Fig. 7.2 shows the variation with time  $t$  of  $V_{IN}$ .

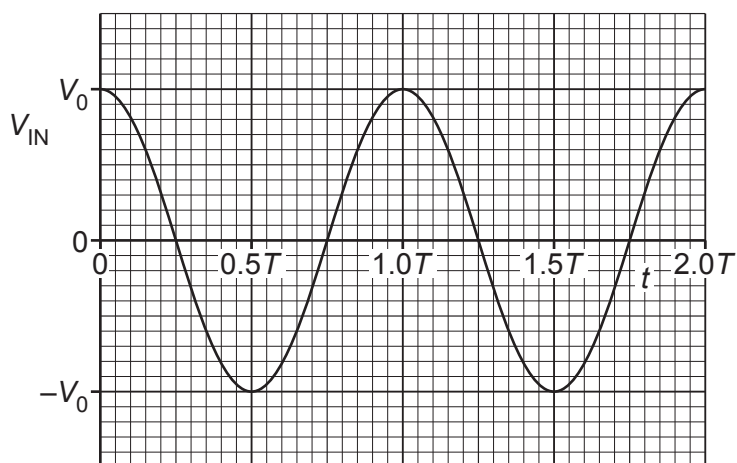

**Fig. 7.2**

- (i) On Fig. 7.3, sketch the variation of  $V_{\text{OUT}}$  with  $t$  between  $t = 0$  and  $t = 2.0T$ .

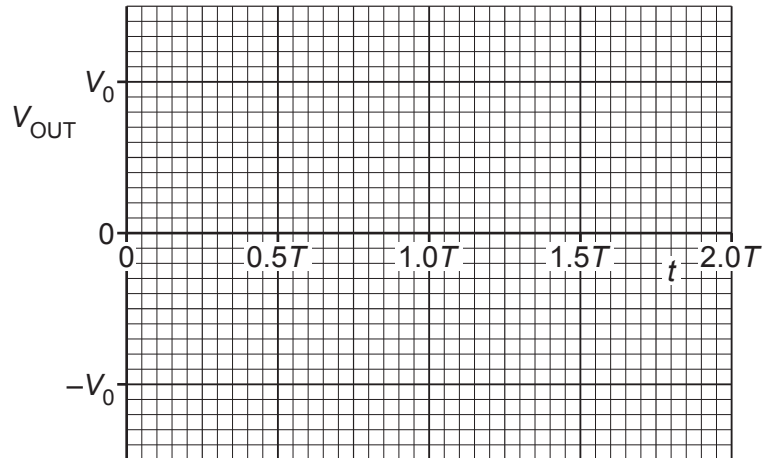


**Fig. 7.3**

[3]

- (ii) The power dissipated in the resistor is  $P$ .

On Fig. 7.4, sketch the variation of  $P$  with  $t$  between  $t = 0$  and  $t = 2.0T$ .

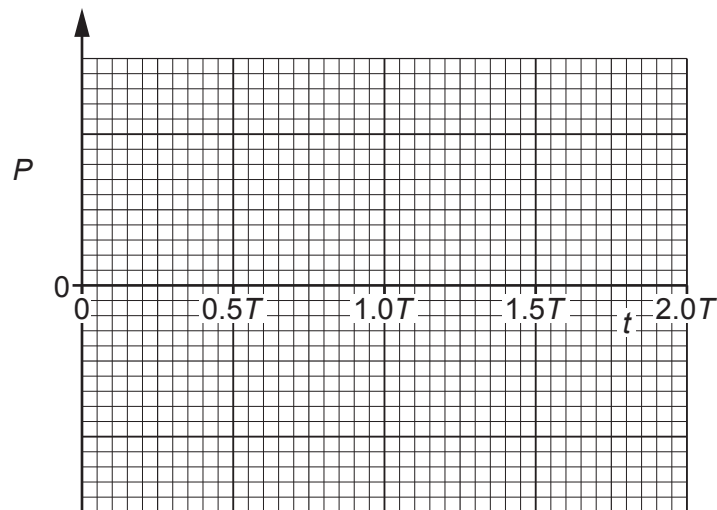

**Fig. 7.4**

[2]

- (iii) Suggest, with a reason, how the root-mean-square (r.m.s.) value of  $V_{\text{OUT}}$  compares with the r.m.s. value of  $V_{\text{IN}}$ .

.....

..... [1]