

- 7 (a) Alternating current (a.c.) is converted into direct current (d.c.) using a full-wave rectification circuit. Part of the diagram of this circuit is shown in Fig. 7.1.

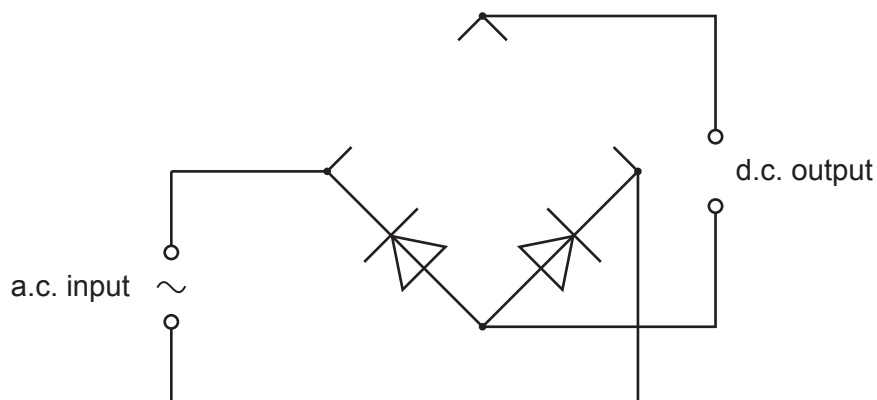


Fig. 7.1

- (i) Complete the circuit in Fig. 7.1 by adding the necessary components in the gaps. [1]
- (ii) On Fig. 7.1 mark with a + the positive output terminal of the rectifier. [1]
- (b) The output voltage  $V$  of an a.c. power supply varies sinusoidally with time  $t$  as shown in Fig. 7.2.

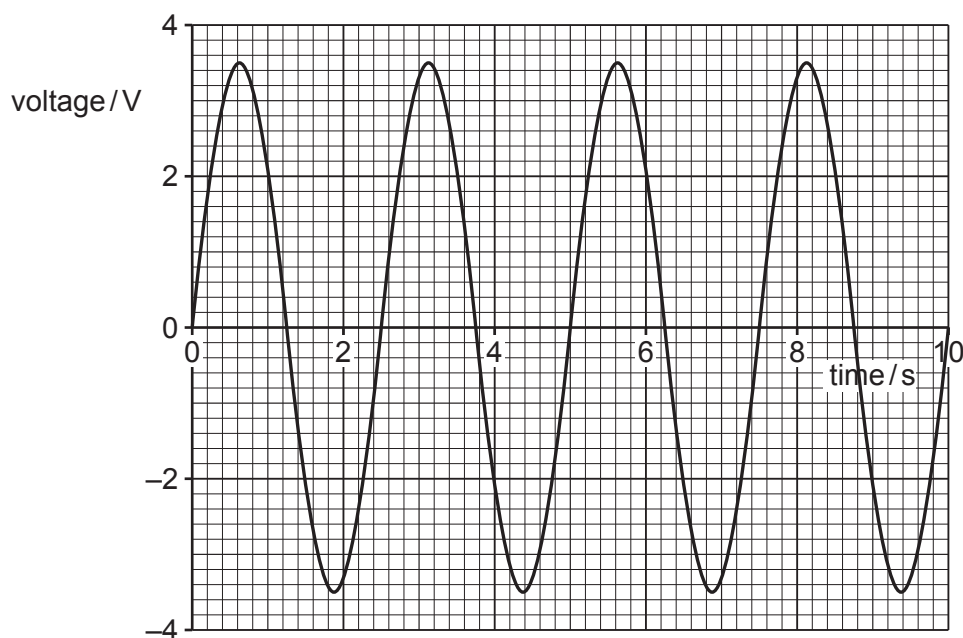


Fig. 7.2

- (i) Determine the equation for  $V$  in terms of  $t$ , where  $V$  is in volts and  $t$  is in seconds.

$V = \dots\dots\dots$  [2]

21

- (ii) The supply is connected to a  $12\Omega$  resistor. Calculate the mean power dissipated in the resistor.

mean power = ..... W [2]