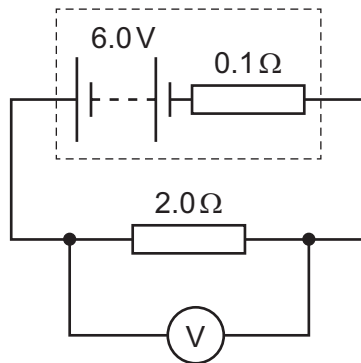


36 The diagram shows a circuit.



What is the reading on the voltmeter?

- A** 0.3V **B** 5.7V **C** 6.0V **D** 6.3V