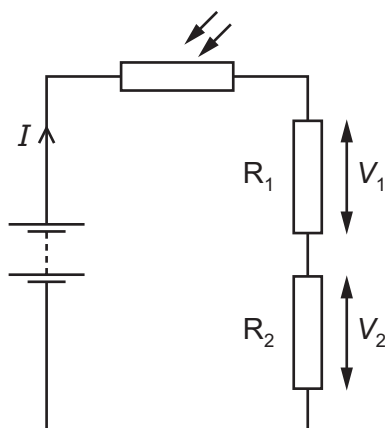


- 34** In the circuit shown, a light-dependent resistor (LDR) is connected to two resistors R_1 and R_2 . The potential difference (p.d.) across R_1 is V_1 and the p.d. across R_2 is V_2 . The current in the circuit is I .



Which statement about this circuit is correct?

- A** The current I increases when the light intensity decreases.
- B** The LDR is an ohmic conductor.
- C** The p.d. V_2 increases when the light intensity decreases.
- D** The ratio $\frac{V_1}{V_2}$ is independent of light intensity.

Space for working