

- 7 (a) Define *electromotive force* (e.m.f.) of a cell.

.....  
 .....[1]

- (b) A cell C of e.m.f. 1.50 V and internal resistance  $0.200\ \Omega$  is connected in series with resistors X and Y, as shown in Fig. 7.1.

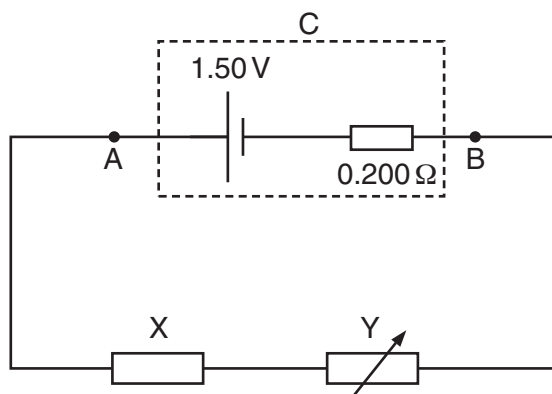


Fig. 7.1

The resistance of X is constant and the resistance of Y can be varied.

- (i) The resistance of Y is varied from 0 to  $8.00\ \Omega$ .

State and explain the variation in the potential difference (p.d.) between points A and B (terminal p.d. across C). Numerical values are not required.

.....  
 .....  
 .....  
 .....[3]

- (ii) The resistance of Y is set at  $6.00\ \Omega$ . The current in the circuit is 0.180 A.

Calculate

1. the resistance of X,

resistance = .....  $\Omega$  [2]

16

2. the p.d. between points A and B,

p.d. = ..... V [2]

3. the efficiency of the cell.

efficiency = .....[2]

[Total: 10]