

32 A student builds the circuit shown. All the lamps are identical.

Which lamp dissipates the most power?

