

- 6 (a) Three resistors of resistances  $R_1$ ,  $R_2$  and  $R_3$  are connected as shown in Fig. 6.1.

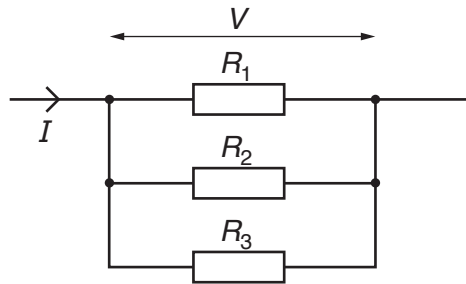


Fig. 6.1

The total current in the combination of resistors is  $I$  and the potential difference across the combination is  $V$ .

Show that the total resistance  $R$  of the combination is given by the equation

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}.$$

[2]

- (b) A battery of electromotive force (e.m.f.)  $6.0\text{ V}$  and internal resistance  $r$  is connected to a resistor of resistance  $12\Omega$  and a variable resistor  $X$ , as shown in Fig. 6.2.

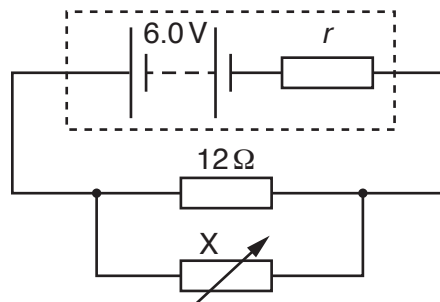


Fig. 6.2

- (i) By considering energy, explain why the potential difference across the battery's terminals is less than the e.m.f. of the battery.

.....

.....

.....

.....[2]

- (ii) A charge of 2.5 kC passes through the battery.

Calculate

1. the total energy transformed by the battery,

energy = ..... J [2]

2. the number of electrons that pass through the battery.

number = ..... [1]

- (iii) The combined resistance of the two resistors connected in parallel is  $4.8\ \Omega$ .

Calculate the resistance of X.

resistance of X = .....  $\Omega$  [1]

- (iv) Use your answer in (b)(iii) to determine the ratio

$$\frac{\text{power dissipated in X}}{\text{power dissipated in } 12\ \Omega \text{ resistor}}.$$

ratio = ..... [2]

- (v) The resistance of X is now decreased. Explain why the power produced by the battery is increased.

.....  
 .....  
 ..... [1]

[Total: 11]