

**33** Which graph could show how the resistance  $R$  of a filament lamp varies with the applied potential difference (p.d.)  $V$ , as  $V$  is increased to the normal operating p.d.?

