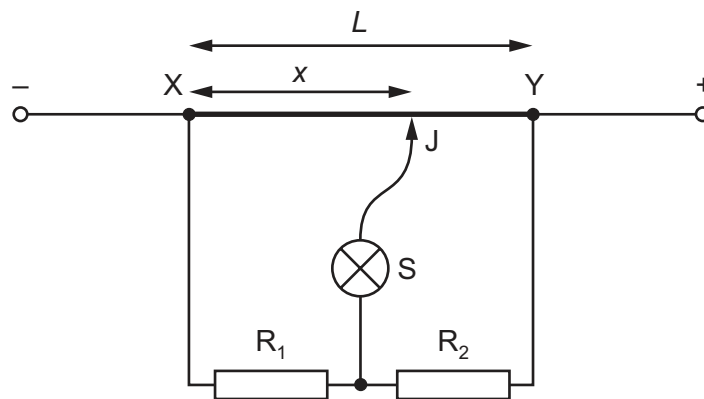


- 38 In the circuit shown, XY is a length  $L$  of uniform resistance wire. A potential difference is applied across XY.  $R_1$  and  $R_2$  are unknown resistors. J is a sliding contact that joins the junction of  $R_1$  and  $R_2$  to points on XY through a lamp S.



J is moved along XY to a point at which the lamp is off. This point is at a distance  $x$  from X.

The potential difference across  $R_1$  is  $V_1$  and the potential difference across  $R_2$  is  $V_2$ .

What is the value of the ratio  $\frac{V_1}{V_2}$ ?

**A**  $\frac{L}{x}$

**B**  $\frac{x}{L}$

**C**  $\frac{L-x}{x}$

**D**  $\frac{x}{L-x}$