

32 Which two units are used to define the coulomb?

A ampere and second

B ampere and volt

C volt and ohm

D volt and second

33 A battery is connected in a circuit with a variable resistor. The potential difference across the variable resistor is 5.50 V.