

- 34** A battery of electromotive force (e.m.f.) 6.0 V and negligible internal resistance is connected to three resistors each of resistance $6.0\ \Omega$.

Which circuit will produce a current through the battery of 0.67 A ?

