

- 32** The potential difference across a metal wire is kept constant. The length  $l$  and the diameter  $d$  of the wire are both varied. The type of metal is kept the same.

How is the current in the wire related to  $l$  and  $d$ ?

- A** It is directly proportional to  $l$  and inversely proportional to  $d$ .
- B** It is directly proportional to  $l$  and inversely proportional to  $d^2$ .
- C** It is inversely proportional to  $l$  and directly proportional to  $d$ .
- D** It is inversely proportional to  $l$  and directly proportional to  $d^2$ .