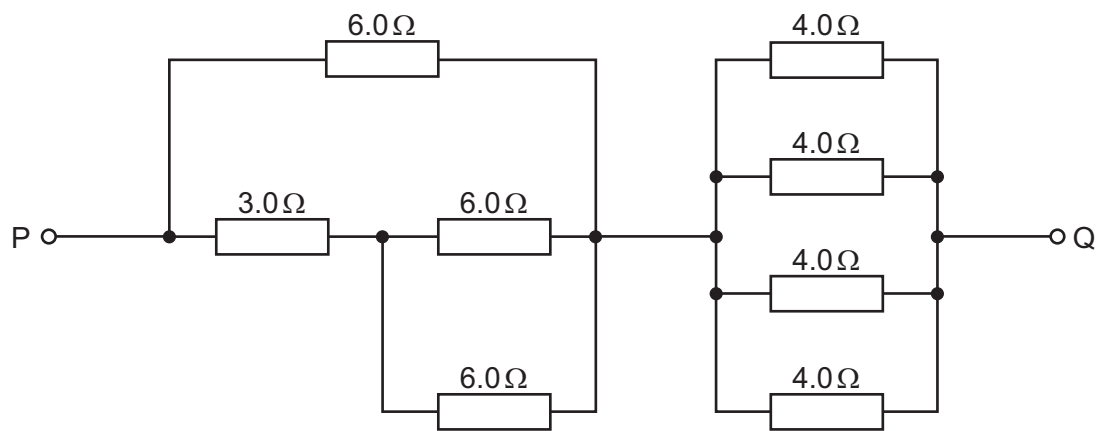


35 The diagram shows part of a circuit.



What is the resistance between the points P and Q due to the resistance network?

- A**  $1.3\Omega$       **B**  $4.0\Omega$       **C**  $10\Omega$       **D**  $37\Omega$

**Space for working**