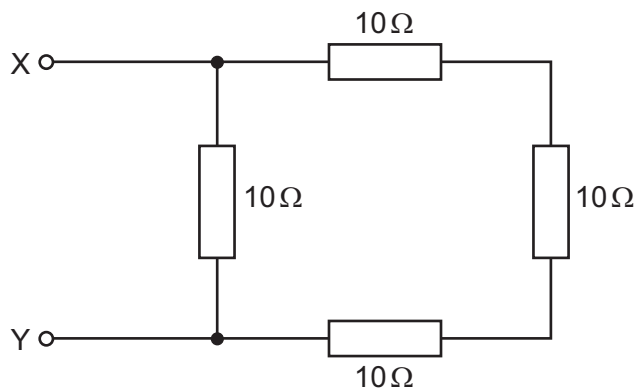


36 The diagram shows an arrangement of resistors.



What is the total electrical resistance between X and Y?

- A** less than $1\ \Omega$
- B** between $1\ \Omega$ and $10\ \Omega$
- C** between $10\ \Omega$ and $30\ \Omega$
- D** $40\ \Omega$

Space for working