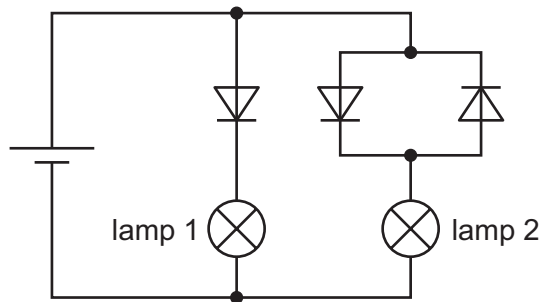


**34** A student assembles the circuit shown.



Which row describes the state of the two lamps?

	lamp 1	lamp 2
<b>A</b>	off	off
<b>B</b>	on	off
<b>C</b>	off	on
<b>D</b>	on	on