

- 7 (a) State two uses of capacitors in electrical circuits, other than for the smoothing of direct current.

1.

2.

[2]

- (b) The combined capacitance between terminals A and B of the arrangement shown in Fig. 7.1 is $4.0 \mu\text{F}$.

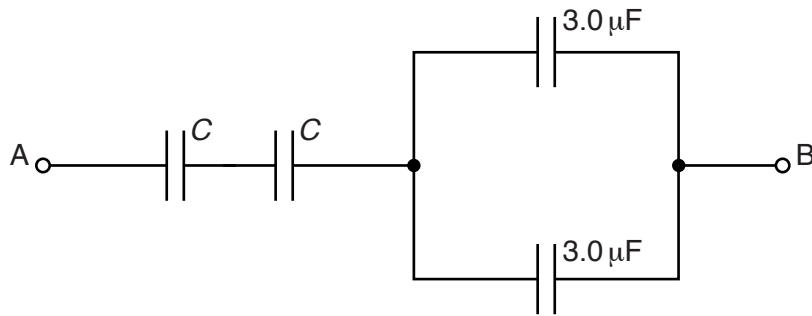


Fig. 7.1

Two capacitors each have capacitance C and the remaining capacitors each have capacitance $3.0 \mu\text{F}$.

The potential difference (p.d.) between terminals A and B is 12 V.

- (i) Determine the capacitance C .

$$C = \dots \mu\text{F} \quad [2]$$

- (ii) Calculate the magnitude of the total positive charge transferred to the arrangement.

$$\text{charge} = \dots \mu\text{C} \quad [2]$$

(iii) Use your answer in (ii) to state the magnitude of the charge on one plate of

1. a capacitor of capacitance C ,

charge = μC

2. a capacitor of capacitance $3.0\ \mu\text{F}$.

charge = μC
[2]

[Total: 8]