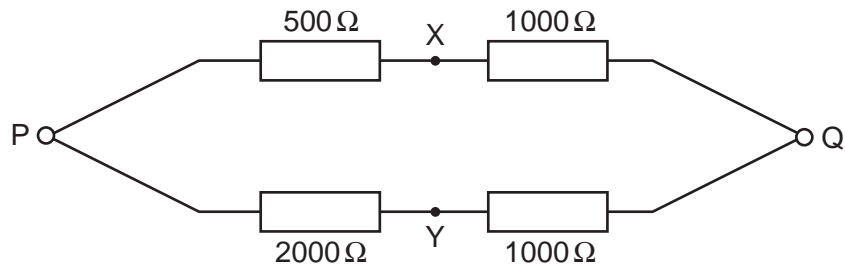


33 A p.d. of 12 V is connected between P and Q.



What is the p.d. between X and Y?

A 0 V

B 4 V

C 6 V

D 8 V