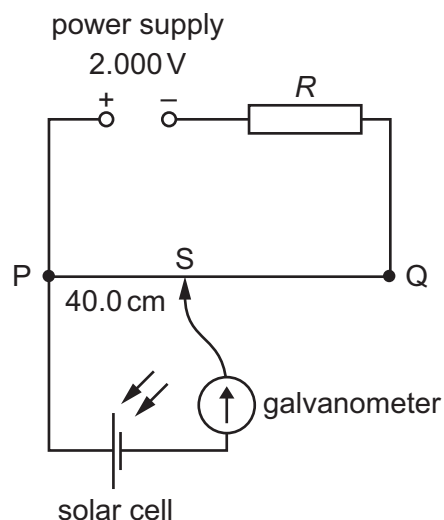


**35** A power supply and a solar cell are compared using the potentiometer circuit shown.



The e.m.f. produced by the solar cell is measured on the potentiometer.

The potentiometer wire PQ is 100.0 cm long and has a resistance of  $5.00\ \Omega$ . The power supply has an e.m.f. of 2.000 V and the solar cell has an e.m.f. of 5.00 mV.

Which resistance  $R$  must be used so that the galvanometer reads zero when  $PS = 40.0\text{ cm}$ ?

- A**  $395\ \Omega$       **B**  $795\ \Omega$       **C**  $995\ \Omega$       **D**  $1055\ \Omega$

**Space for working**