

6 (a) (i) Define the *capacitance* of a parallel plate capacitor.

.....

.....

..... [2]

(ii) State **three** functions of capacitors in electrical circuits.

1. ....
  2. ....
  3. ....
- [3]

(b) A student has available **three** capacitors, each of capacitance  $12\mu\text{F}$ .

Draw diagrams, one in each case, to show how the student connects the capacitors to give a combined capacitance between the terminals of:

(i)  $18\mu\text{F}$



[1]

(ii)  $8\mu\text{F}$ .



[1]