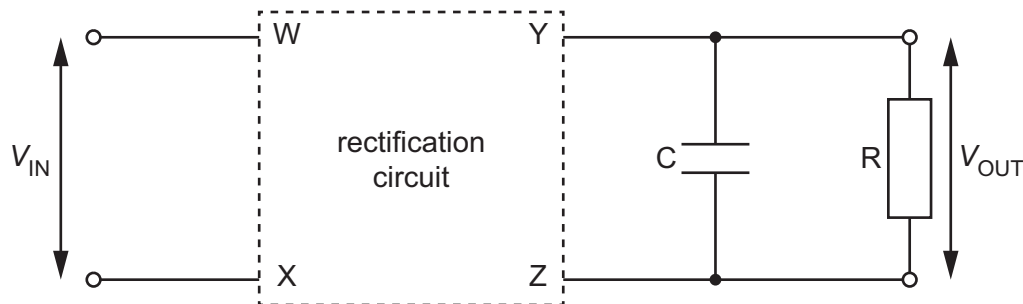


- 6 Fig. 6.1 shows a circuit that rectifies an alternating input voltage  $V_{IN}$  and produces an output voltage  $V_{OUT}$  across a resistor  $R$ .



**Fig. 6.1**

The four terminals of the rectification circuit are labelled W, X, Y and Z.  
A capacitor  $C$  is connected in parallel with resistor  $R$ .


- (a) (i) State what is meant by rectification.

.....  
..... [1]

- (ii) State the purpose of capacitor  $C$ .

.....  
..... [1]

- (b) Fig. 6.2 shows the variations with time  $t$  of the potential differences (p.d.s)  $V_{IN}$  and  $V_{OUT}$ .

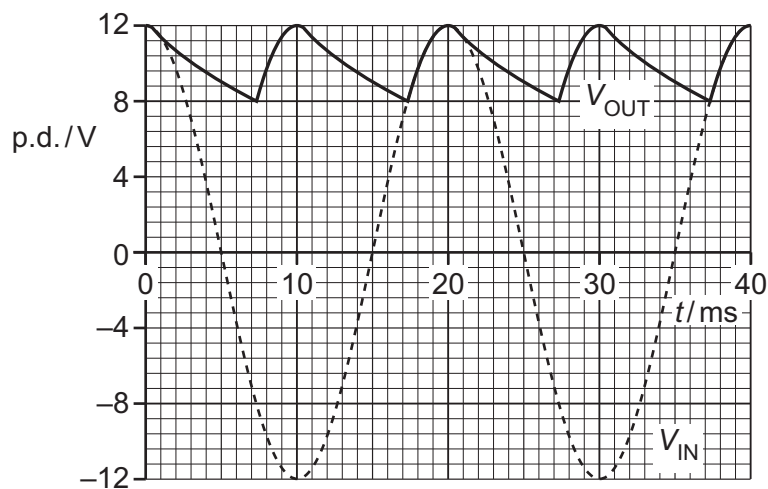

**Fig. 6.2**



- (i) The variation of  $V_{\text{IN}}$  with  $t$  can be represented by

$$V_{\text{IN}} = A \cos Bt$$

where  $A$  and  $B$  are constants.

Determine the values of  $A$  and  $B$ . Give a unit with your answer for  $A$ .

$$A = \dots\dots\dots \text{unit} \dots\dots\dots$$

$$B = \dots\dots\dots \text{rad s}^{-1} \quad [2]$$

- (ii) Determine the type of rectification produced by the circuit in Fig. 6.1.

..... [1]

- (iii) On Fig. 6.3, draw the circuit diagram for the components inside the rectification circuit.

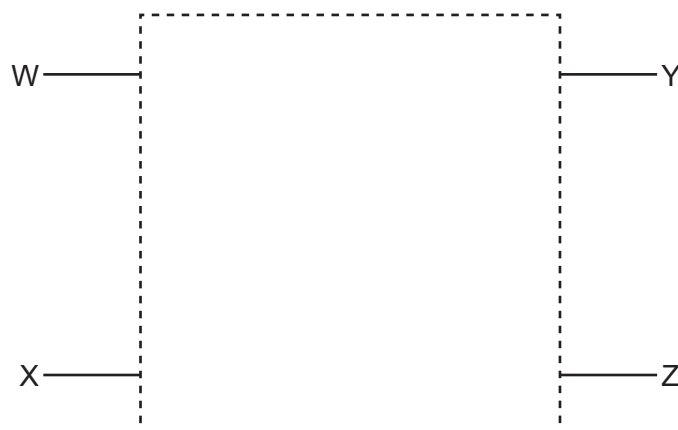


Fig. 6.3

[2]

- (iv) Determine a value for the time constant for the discharge of the capacitor  $C$  through the resistor  $R$  in Fig. 6.1.

time constant = ..... s [3]



\* 0000800000014 \*

DFD



14

(c) The capacitor C has a capacitance of  $570\ \mu\text{F}$ .

Use your answer in **(b)(iv)** to determine the resistance of resistor R.

resistance = .....  $\Omega$  [2]

[Total: 12]